

```
timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/13/2022 09:35:17 PM
// Design Name:
// Module Name: Lab3_sim
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
```

```
module Lab3_sim();
wire [6:0] seg;
wire dp;
wire [3:0] an;
reg [7:0]sw;
reg btnC, btnL, clkIn, btnR;
wire [7:0] D7Seg3, D7Seg2, D7Seg1, D7Seg0;

Top_level UUT(
    .sw(sw[7:0]), .btnL(btnL), .btnC(btnC), .btnR(btnR), .clkIn(clkIn),
    .seg(seg[6:0]), .dp(dp),
    .an(an[3:0])
);

show_7segDisplay showit (
    .seg(seg[6:0]),
    .DP(dp), .AN0(an[0]), .AN1(an[1]), .AN2(an[2]), .AN3(an[3]),
    .D7Seg0(D7Seg0), .D7Seg1(D7Seg1), .D7Seg2(D7Seg2), .D7Seg3(D7Seg3)
);
```

```

parameter PERIOD = 10;
    parameter real DUTY_CYCLE = 0.5;
    parameter OFFSET = 2;

initial    // Clock process for clkin
begin
    #OFFSET
        clkin = 1'b1;
    forever
        begin
            #(PERIOD-(PERIOD*DUTY_CYCLE)) clkin = ~clkin;
        end
    end
end

initial
begin
    btnR = 1'b0;
    #50;
    sw = 8'b00000000;
    btnL = 1'b0;
    btnC = 1'b0;

    #50;
    sw = 8'b00010001;
    // shows 1 1
    #50;
    sw = 8'b00100010;
    // shows 2 2
    #50;
    sw = 8'b00110011;
    //shows 3 3
    #50;
    sw = 8'b01000100;
    //shows 4 4
    #50;
    sw = 8'b01010101;
    //shows 5 5
    #50;
    sw = 8'b01100110;
    // shows 6 6
    #50;
    sw = 8'b01110111;
    // shows 7 7
    #50;
    sw = 8'b10001000;
    // shows      8 8

```

```

#50;
sw = 8'b10011001;
//shows 9 9
#50;
sw = 8'b10101010;
//shows A A (10 10)
#50;
sw = 8'b10111011;
//shows b b (11 11)
#50;
sw = 8'b11001100;
//shows C C (12 12)
#50;
sw = 8'b11111101;
// shows F D (15 13)
#50;
sw = 8'b01101001;
// shows 6 9 (ha nice)
#50;
sw = 8'b01000010;
// shows 4 2
#50;
sw = 8'b10000000;
//shows 8 0
#50;
end
endmodule

module show_7segDisplay (
    input [6:0] seg,
    input DP,AN0,AN1,AN2,AN3,
    output reg [7:0] D7Seg0, D7Seg1, D7Seg2,D7Seg3);

    reg [7:0] val;

    always @(AN0 or val)
    begin
        if (AN0 == 0) D7Seg0 <= val;
        else if (AN0 == 1) D7Seg1 <= " ";
        else D7Seg0 <= 8'bX;    // non-blocking assignment
    end

    always @(AN1 or val)
    begin
        if (AN1 == 0) D7Seg1 <= val;
        else if (AN1 == 1) D7Seg1 <= " ";
        else D7Seg1 <= 8'bX;    // non-blocking assignment
    end

```

```

end

always @(AN2 or val)
begin
    if (AN2 == 0) D7Seg2 <= val;
    else if (AN2 == 1) D7Seg2 <= " ";
    else D7Seg2 <= 8'bX;    // non-blocking assignment
end

always @(AN3 or val)
begin
    if (AN3 == 0) D7Seg3 <= val;
    else if (AN3 == 1) D7Seg3 <= " ";
    else D7Seg3 <= 8'bX;    // non-blocking assignment
end

always @(seg)
case (seg)
7'b01111111:
    val = "-";
7'b11111111:
    val = " ";
7'b10000000:
    val = "0";
7'b1111001:
    val = "1";
7'b0100100:
    val = "2";
7'b0110000:
    val = "3";
7'b0011001:
    val = "4";
7'b0010010:
    val = "5";
7'b0000010:
    val = "6";
7'b1111000:
    val = "7";
7'b0000000:
    val = "8";
7'b0011000:
    val = "9";
7'b0001000:
    val = "A";
7'b0000011:
    val = "B";

```

```
7'b1000110:
    val = "C";
7'b0100001:
    val = "D";
7'b0000110:
    val = "E";
7'b0001110:
    val = "F";
default:
    val = 8'bX;
endcase
endmodule
```