

```

timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/27/2022 01:57:14 PM
// Design Name:
// Module Name: countUD4L
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

```

```

module countUD4L(
    input clk,
    input Up,
    input Dw,
    input LW,
    input [3:0] d,

    output [3:0] q,
    output UTC,
    output DTC

);
//upper is active when all are 1
assign UTC = (q[3] & q[2] & q[1] & q[0]);
//lower active when all are 0
assign DTC = (~q[3] & ~q[2] & ~q[1] & ~q[0]);

wire [3:0] out;
wire [3:0] Upcnt;
wire [2:0] Downcnt;
wire cloud;

// making all the logic for the up and down count for the cloud

```

```

// broke down the logic into pieces to be easier to define
assign cloud = (Up ^ Dw) | LW;
// up count logic made to define the flip flops easier later which is FDRE
assign Upcnt[0] = (q[0] ^ cloud);
assign Upcnt[1] = q[1] ^ (cloud & q[0]);
assign Upcnt[2] = q[2] ^ (cloud & q[1] & q[0]);
assign Upcnt[3] = q[3] ^ (cloud & q[1] & q[2] & q[0]);
// down count logic which is upcount but inversed
assign Downcnt[0] = q[1] ^ (cloud & ~q[0]);
assign Downcnt[1] = q[2] ^ (cloud & ~q[1] & ~q[0]);
assign Downcnt[2] = q[3] ^ (cloud & ~q[2] & ~q[1] & ~q[0]);

//logic for the outputs of all the flip flops (4 bit flipflop)
assign out[3] = (((Upcnt[3] & Up & ~Dw) | (Downcnt[2] & ~Up & Dw)) & ~LW) | (LW
& d[3]));
assign out[2] = (((Upcnt[2] & Up & ~Dw) | (Downcnt[1] & ~Up & Dw)) & ~LW) | (LW
& d[2]));
assign out[1] = (((Upcnt[1] & Up & ~Dw) | (Downcnt[0] & ~Up & Dw)) & ~LW) | (LW
& d[1]));
assign out[0] = (((Upcnt[0] & Up & ~Dw) | (Upcnt[0] & ~Up & Dw)) & ~LW) | (LW &
d[0]));

FDRE #(.INIT(1'b0) ) flip3 (.C(clk), .CE(cloud), .D(out[3]), .Q(q[3]));
FDRE #(.INIT(1'b0) ) flip2 (.C(clk), .CE(cloud), .D(out[2]), .Q(q[2]));
FDRE #(.INIT(1'b0) ) flip1 (.C(clk), .CE(cloud), .D(out[1]), .Q(q[1]));
FDRE #(.INIT(1'b0) ) flip0 (.C(clk), .CE(cloud), .D(out[0]), .Q(q[0]));

endmodule

```